
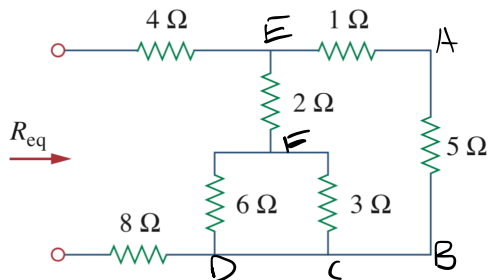


Find equivalent resistance

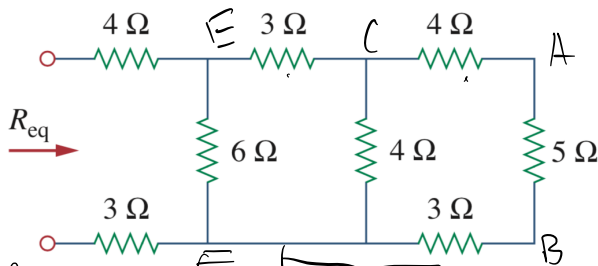


$$R_{eq} = 8 + 4 + 2 \cdot 4 = 14.4 \Omega$$

Find equivalent resistance




$$R_{eq} = 4 + 3 + 3 = 10 \Omega$$

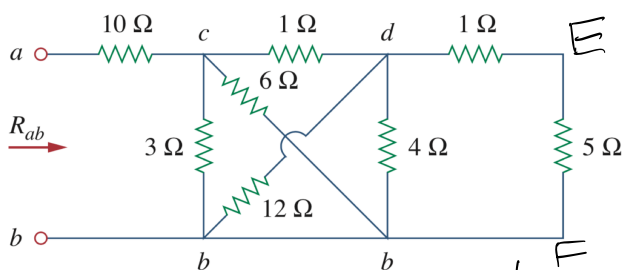

$$R_{ab} = 10 + \left(\frac{1}{3} + \frac{1}{6} + \frac{1}{3} \right)^{-1} = 11.2 \Omega$$

Find equivalent resistance

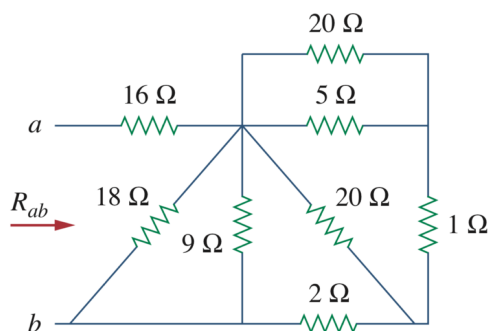

$$R_{ab} = 16 + \left(\frac{1}{18} + \frac{1}{3 \cdot 6} \right)^{-1} = 19 \Omega$$

