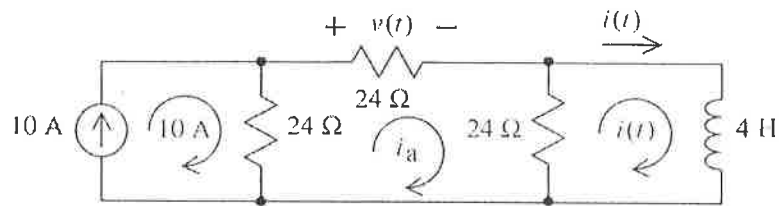


P7.5-13



15pt

We'll write and solve a mesh equation. Label the meshes as shown. Apply KVL to the center mesh to get

$$24i_a + 24(i_a - i(t)) + 24(i_a - 10) = 0 \Rightarrow i_a = \frac{i(t) + 10}{3} = 5 - e^{-4t} \text{ A for } t > 0$$

Then



$$v(t) = 24i_a = 120 - 24e^{-4t} \text{ V for } t > 0$$

5pt.

(checked: LNAP 6/25/04)

15

P8.3-25

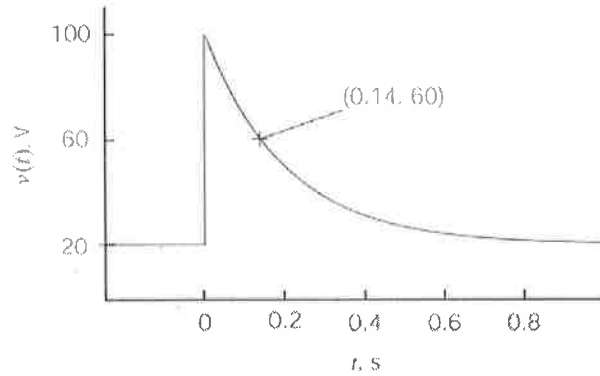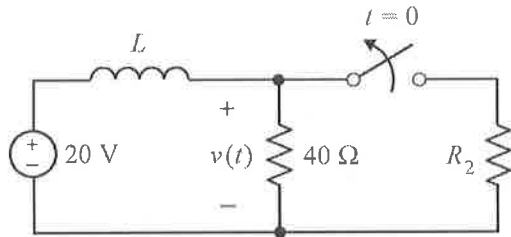

From the plot $D = v(t)$ for $t < 0 = 20$ V, $E + F = v(0+) = 100$ V and $E = \lim_{t \rightarrow \infty} v(t) = 20$ V. The point labeled on the plot indicates that $v(t) = 60$ V when $t = 0.14$ s. Consequently

$$60 = 20 + 80e^{-a(0.14)} \Rightarrow a = \frac{\ln\left(\frac{60-20}{80}\right)}{-0.14} = 5 \frac{1}{s}$$

Then

$$v(t) = \begin{cases} 20 \text{ V} & \text{for } t \leq 0 \\ 20 + 80e^{-5t} \text{ V} & \text{for } t \geq 0 \end{cases}$$

At $t = 0+$,



$$i(0+) = \frac{100}{40} = 2.5 \text{ A}$$

When $t < 0$, the circuit is at steady state so the inductor acts like a short circuit.

$$40 \parallel R_2 = \frac{20}{2.5} = 8 \Omega \Rightarrow R_2 = 10 \Omega$$

Next, the inductance can be determined using the time constant:

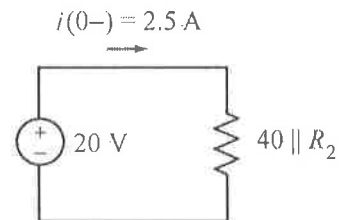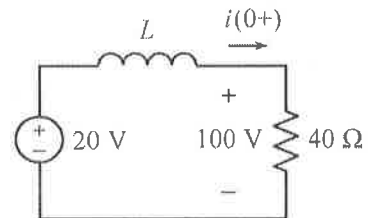
$$5 = a = \frac{1}{\tau} = \frac{40}{L} \Rightarrow L = \frac{40}{5} = 8 \text{ H}$$



20pt

P8.7-1

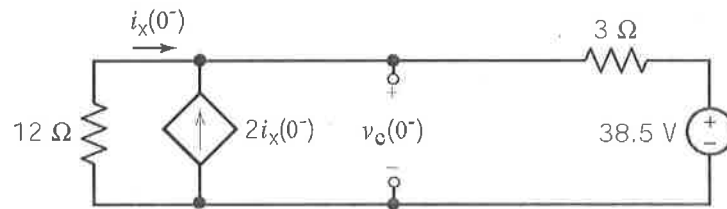
Assume that the circuit is at steady state before $t = 0$:



$$\text{KVL : } 12i_x + 3(3i_x) + 38.5 = 0 \Rightarrow i_x = -1.83 \text{ A}$$

$$\text{Then } v_c(0^-) = -12i_x = 22 \text{ V} = v_c(0^+)$$

After $t = 0$:

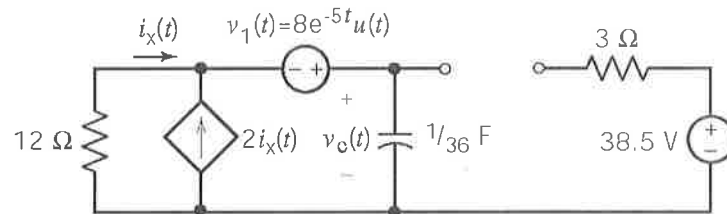

$$\text{KVL : } 12i_x(t) - 8e^{-5t} + v_c(t) = 0$$

$$\text{KCL : } -i_x(t) - 2i_x(t) + (1/36) \frac{dv_c(t)}{dt} = 0 \Rightarrow i_x(t) = \frac{1}{108} \frac{dv_c(t)}{dt}$$

$$\therefore 12 \left[\frac{1}{108} \frac{dv_c(t)}{dt} \right] - 8e^{-5t} + v_c(t) = 0$$

$$\frac{dv_c(t)}{dt} + 9v_c(t) = 72e^{-5t} \Rightarrow v_{cn}(t) = Ae^{-9t}$$

$$\text{Try } v_{cf}(t) = Be^{-5t} \text{ \& substitute into the differential equation } \Rightarrow B = 18$$

$$\therefore v_c(t) = Ae^{-9t} + 18e^{-5t}$$

$$v_c(0) = 22 = A + 18 \Rightarrow A = 4$$

$$\therefore v_c(t) = 4e^{-9t} + 18e^{-5t} \text{ V}$$