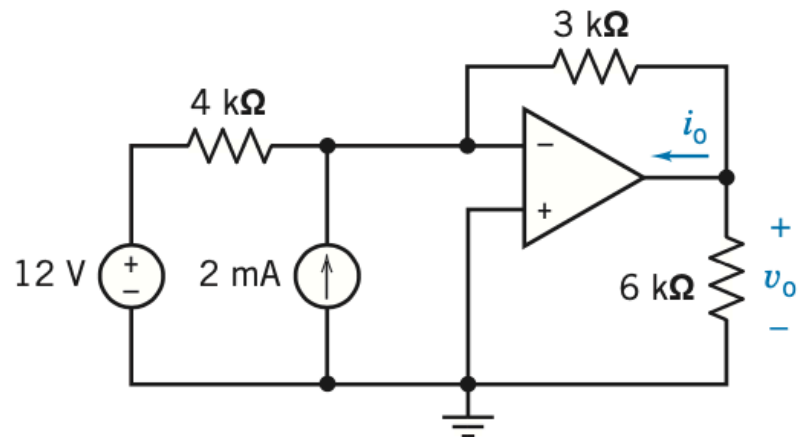


Name:

Problem#1 (10 Points) (Hint - Ideal Op Amp)


Find v_o and i_o for the circuit of Figure



Name:

Problem #2 (10 Points) (Hint - Node Analysis with Ideal Op Amp)


Find v_o and i_o for the circuit of

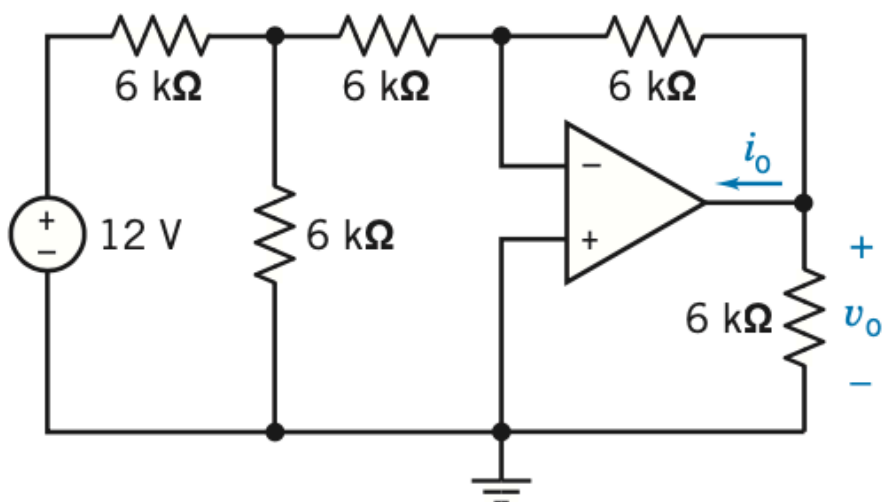

Name:

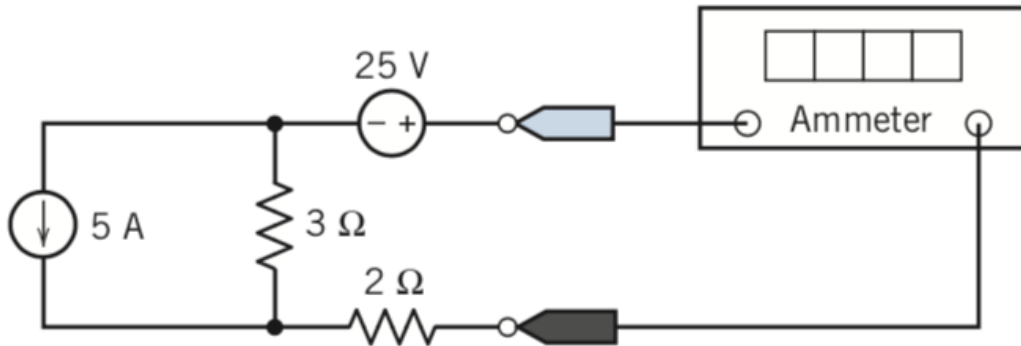Problem #3 (10 Points)


Using Superposition principle, find the value of current measured by ammeter in figure below.



Name:

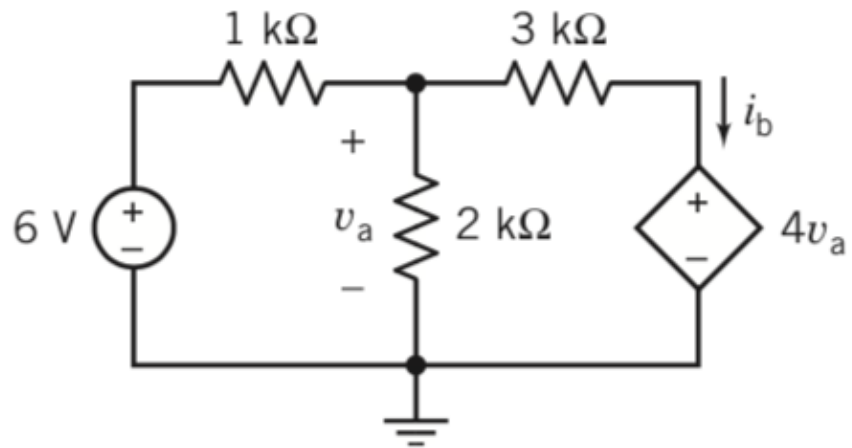Problem #4 (10 points)

Find the current i_b in the circuit below



Name:

Problem #5 (10 points)

For the circuit shown below, use Norton's theorem to formulate a general expression for current i in terms of resistance R .

